

CS220A Lab#2

Adders and Comparators

Mainak Chaudhuri
Indian Institute of Technology Kanpur

Sketch

- Assignment#1: two-bit adder
- Assignment#2: seven-bit adder
- Assignment#3: eight-bit comparator

Lab#2

- Make new folders Lab2_1, Lab2_2, Lab2_3 under CS220Labs to do the assignments
- Refer to lab#1 slides for Xilinx ISE instructions
- Finish pending assignments from lab#1 first
- Assignment marks:
 - Assignment#1: 2 marks
 - Assignment#2: 4 marks
 - Assignment#3: 5 marks

Assignment#1

- Assignment#1
 - Design a two-bit adder with cin of the least significant bit adder assumed to be zero
 - Total number of inputs is four: $x[0]$, $x[1]$, $y[0]$, $y[1]$
 - Three outputs: $z[0]$, $z[1]$, and carry from the most significant bit adder
 - $z = x + y$
 - Use SW0 and SW1 to feed $x[0]$ and $x[1]$
 - Use SW2 and SW3 to feed $y[0]$ and $y[1]$
 - Observe $z[1]$ and $z[0]$ in LED1 and LED0
 - Observe carry in LED2

Assignment#1

- Write a Verilog module for a full adder
- Write a Verilog module that instantiates two full adder modules and connects them appropriately to design the two-bit adder
- Write a top-level Verilog Test Fixture for simulation
- Simulate and synthesize your design

Assignment#1

- Verilog module for two-bit adder

```
module two_bit_adder (x, y, z, carry);  
    input [1:0] x;  
    input [1:0] y;  
    output [1:0] z;  
    wire [1:0] z;  
    output carry;  
    wire carry;  
    wire carry0;  
    full_adder FA0 (x[0], y[0], 1'b0, z[0], carry0);  
    full_adder FA1 (x[1], y[1], carry0, z[1], carry);  
endmodule
```

Assignment#2

- Seven-bit adder
 - Only four slide switches on board, but need to input two seven-bit numbers
 - Idea is to divide each input (say, A and B) into two halves and use the four push buttons
 - Place the slide switches in position for the lower four bits of A and push one of the push buttons PB1 (say, BTN_NORTH)
 - Place the slide switches in position for the higher three bits of A and push another push button PB2 (say, BTN_SOUTH)
 - The Verilog module should be written such that when PB1's posedge comes, A[3:0] is stored and when PB2's posedge comes, A[6:4] is stored
 - Input B using the remaining two push buttons

Assignment#2

- Push buttons
 - Read pages 16 and 17 from https://www.xilinx.com/support/documentation/boards_and_kits/ug230.pdf
 - We will use BTN_EAST, BTN_WEST, BTN_SOUTH, and BTN_NORTH along with the slide switches for feeding the inputs in this assignment
 - The seven-bit sum and carry-out should be shown on the eight LEDs
 - LED0 should be sum[0], ..., LED6 should be sum[6], and carry-out should be LED7

Assignment#2

- Plan the Verilog modules
 - 1st level: a full adder module that can add two bits with a carry-in
 - 2nd level: an array of seven full adders in ripple-carry mode (carry-in of LSB should be set to 0)
 - Inputs: PB1, PB2, PB3, PB4, Y where Y is a four-bit number; four bits of Y are the slide switch inputs
 - Outputs: seven-bit sum and carry-out
 - Structure:
 - Four always blocks, one each for posedge PB1/2/3/4; sequential assignment for A[3:0], A[6:4], B[3:0], B[6:4] in the always blocks (one assignment per always block); for example, A[3:0] <= Y; A[6:4] <= Y[2:0];
 - Array of seven full adders (outside always blocks)

Assignment#2

- Write a suitable Verilog Test Fixture for ISim simulation
- Run PlanAhead to assign pins to inputs and outputs
 - Make sure to use exactly same IOSTANDARD, PULLUP/PULLDOWN, SLEW, DRIVE for the pins as shown in Chapter 2 of https://www.xilinx.com/support/documentation/boards_and_kits/ug230.pdf
 - Manually add the following in the .ucf file
 - NET "PB1" CLOCK_DEDICATED_ROUTE = FALSE;
 - Same for PB2, PB3, PB4
- Synthesize the seven-bit adder on FPGA

Assignment#3

- Eight-bit comparator
 - Compares two eight-bit inputs A and B
 - Outputs whether $A < B$, $A > B$, $A == B$
 - Accept inputs same way as the previous assignment
 - LED0 should glow if $A < B$, LED1 should glow if $A > B$, LED2 should glow if $A == B$

Assignment#3

- Verilog modules
 - Decompose the eight-bit comparator as follows
 - Number the bit positions 0 to 7 from LSB to MSB
 - Focus on bit position k comparing a_k and b_k
 - Start comparing from MSB and the first bit position where $a_k \neq b_k$ decides whether $A < B$ or $A > B$; this observation leads to the first level module
 - 1st level: inputs are two bits (a , b) to be compared and less, greater, equal indication from the next MSB position
 - If the less input is 1, the output is less irrespective of a , b
 - If the greater input is 1, the output is greater irrespective of a , b
 - If equal input is 1, output is $a < b$, $a > b$, or $a == b$

Assignment#3

- Verilog modules
 - 2nd level
 - Array of eight 1st level comparators
 - The equal input of MSB comparator should be 1 and the less, greater inputs should be 0
 - The outputs of the LSB comparator are the final outputs
- Write a Verilog Test Fixture with appropriate inputs for ISim
- Use PlanAhead to assign pins and synthesize your hardware on FPGA
 - Manually add the following in the .ucf file
 - NET "PB1" CLOCK_DEDICATED_ROUTE = FALSE;
 - Same for PB2, PB3, PB4