


Types of Digital Logic Circuits:

- * **Combinational (or Combinatorial)**
- * **Sequential**

Combinational Circuit:

- * Consists of *logic gates* whose outputs at any time are determined by the *present* combination of inputs
- * Performs an operation specified *logically* by a set of *Boolean functions*
- * Has *input variables*, *logic gates*, and *output variables*
- * **Logic gates accept signals from inputs and generate signals to outputs**

 - * **Transforms binary information from given input data to required output data**



- * *For n i/p variables, 2^n possible binary i/p combinations*
- * *For each possible i/p combination, there is one possible o/p value*
 - \Rightarrow Can be represented by a ***Truth Table***
 - \Rightarrow Can also be described by m ***Boolean functions***, one for each o/p variable
 - \Rightarrow ***Each o/p function is expressed in terms of n i/p variables***

*** *Examples:***

- **Adders**
- **Subtractors**
- **Multipliers**
- **Comparators**
- **Decoders**
- **Encoders**
- **Multiplexers (*MUX*)**
- **De-Multiplexers (*De-MUX*)**

Sequential Circuit:

- * Employ *storage elements* in addition to *logic gates*
- * O/ps function of i/ps and *state* of these storage elements
- * State of storage elements function of *previous i/ps*
- * *O/ps depend not only on present values of i/ps, but also on past i/ps*
- * Circuit behavior must be specified by a *time sequence* of *i/ps* and *internal states*

How to identify a Combinational Circuit ?

- * Would have *only logic gates* with *no feedback paths or memory elements*
- * **Feedback paths immediately denote sequential circuits**

Adder:

- * $0 + 0 = 0$, $0 + 1 = 1$, $1 + 0 = 1$, $1 + 1 = 10$
- * First three cases have *sums* of 0 or 1, but no *carry* (or *0 carry*)
- * Fourth case has a *carry* of 1, which should be *added* to the next 2 significant bits
- * *Simple addition of 2 bits* → **Half Adder (HA)**
- * *Addition of 3 bits (2 significant bits and 1 carry)*
→ **Full Adder (FA)**
- * **Note: 2 HAs can be used to implement a FA**


Half Adder (HA):

* *2 binary i/ps and 2 binary o/ps* [**Sum (S)** and **Carry (C)**]

* Thus, $0 + 0 = 0$ (S) and 0 (C), $0 + 1 = 1$ (S) and 0 (C),
 $1 + 0 = 1$ (S) and 0 (C), $1 + 1 = 0$ (S) and 1 (C)

* Thus, it can be clearly seen that for i/ps X and Y:
 
$$S = X \oplus Y = X'Y + XY', \text{ and } C = XY$$



Full Adder (FA):

* **Arithmetic sum of 3 bits: 3 i/ps** (X, Y, and C_{in}) and **2 o/ps** (S and C_{out})

X \ YC_{in}				
	00	01	11	10
0	0 ⁰	1 ¹	3 ⁰	2 ¹
1	4 ¹	5 ⁰	7 ¹	6 ⁰

K-Map for S

$$S = X'Y'C_{in} + X'YC'_{in} + XY'C'_{in} + XYC_{in}$$

X \ YC_{in}				
	00	01	11	10
0	0 ⁰	1 ⁰	3 ¹	2 ⁰
1	4 ⁰	5 ¹	7 ¹	6 ¹

K-Map for C_{out}

$$C_{out} = XC_{in} + XY + YC_{in}$$

X	Y	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Optimization:


$$\begin{aligned}
 * \text{ Note: } S &= XYC_{in} + X'Y'C_{in} + XY'C'_{in} + X'YC'_{in} \\
 &= C_{in}(XY + X'Y') + C'_{in}(XY' + X'Y) \\
 &= C_{in}(X \oplus Y)' + C'_{in}(X \oplus Y) \\
 &= C_{in} \oplus (X \oplus Y)
 \end{aligned}$$

		YC _{in}			
		00	01	11	10
X	0	⁰ 0	¹ 0	³ 1	² 0
	1	⁴ 0	⁵ 1	⁷ 1	⁶ 1

* Alternate K-map for C_{out} yields:

$$\begin{aligned}
 C_{out} &= XY'C_{in} + X'YC_{in} + XY \\
 &= C_{in}(XY' + X'Y) + XY \\
 &= C_{in}(X \oplus Y) + XY
 \end{aligned}$$

Implementation:

 


* $S = C_{in} \oplus (X \oplus Y)$ and $C_{out} = C_{in} (X \oplus Y) + XY$

* **Note: A Full Adder can be constructed using two Half Adders and an OR gate**

Binary Adder:

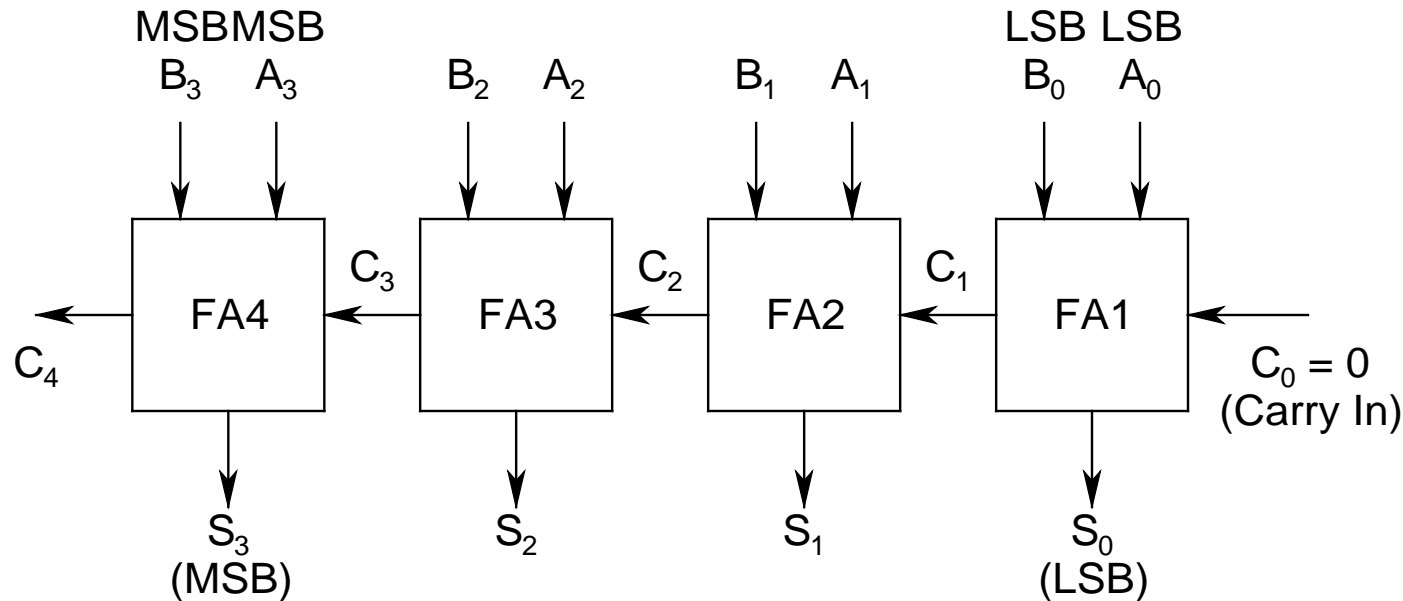- * Performs *arithmetic sum* of two binary numbers ($B_3B_2B_1B_0$ and $A_3A_2A_1A_0$) and provides *Sum* ($S_3S_2S_1S_0$) and *Carry Out* (C_4)




4-Bit Adder

- * FAs *connected in cascade*, with the o/p carry from each FA connected to the i/p carry of the next FA
- * Also known as **Ripple Carry Adder**
- * **Limitation: Gate Delay :**
 - S_0 and C_1 generated first, then S_1 and C_2 , then S_2 and C_3 , and finally S_3 and C_4
 - \Rightarrow Thus, all o/ps will be **valid** only after **4 gate delays**
 - \Rightarrow This is known as the **Carry Propagation Problem**

Binary Subtractor:

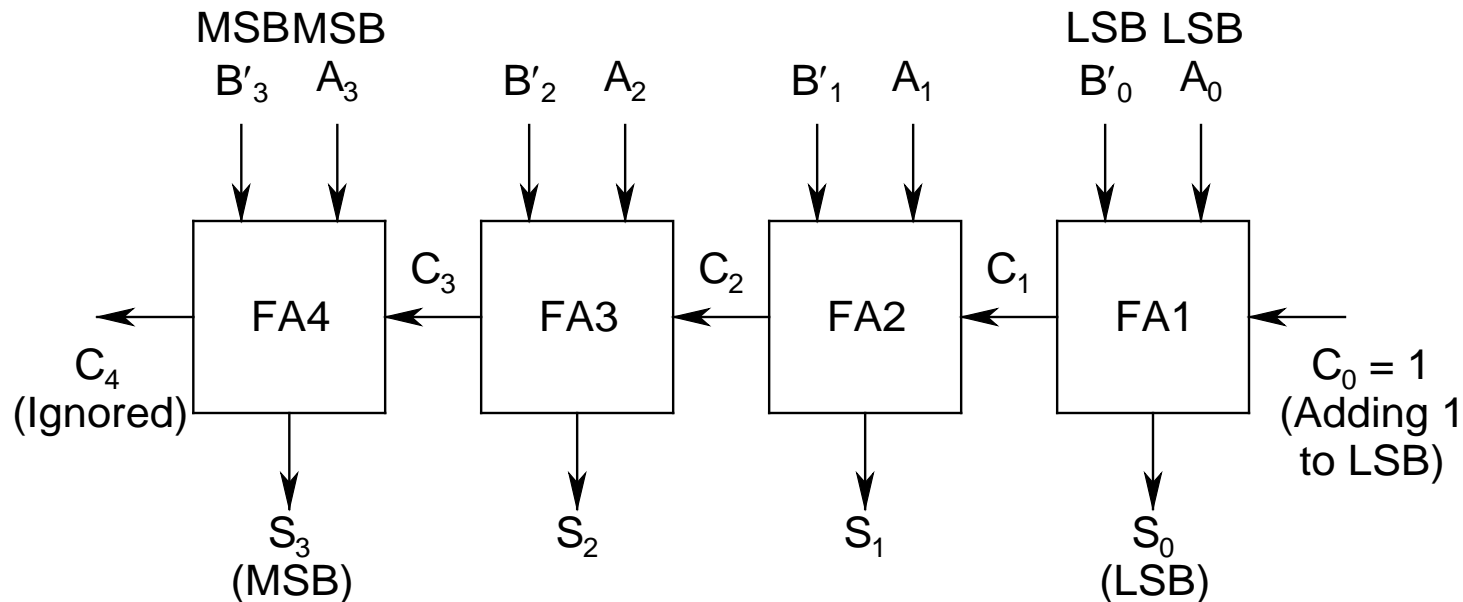
- * **Recall:** Subtraction is *equivalent* to adding two numbers, with the number to be subtracted expressed in *2's complement notation*
- * **2's complement:** Invert all bits and add 1 to LSB



4-Bit Subtractor (Subtracting $B_3B_2B_1B_0$ from $A_3A_2A_1A_0$)

Binary Adder/Subtractor:

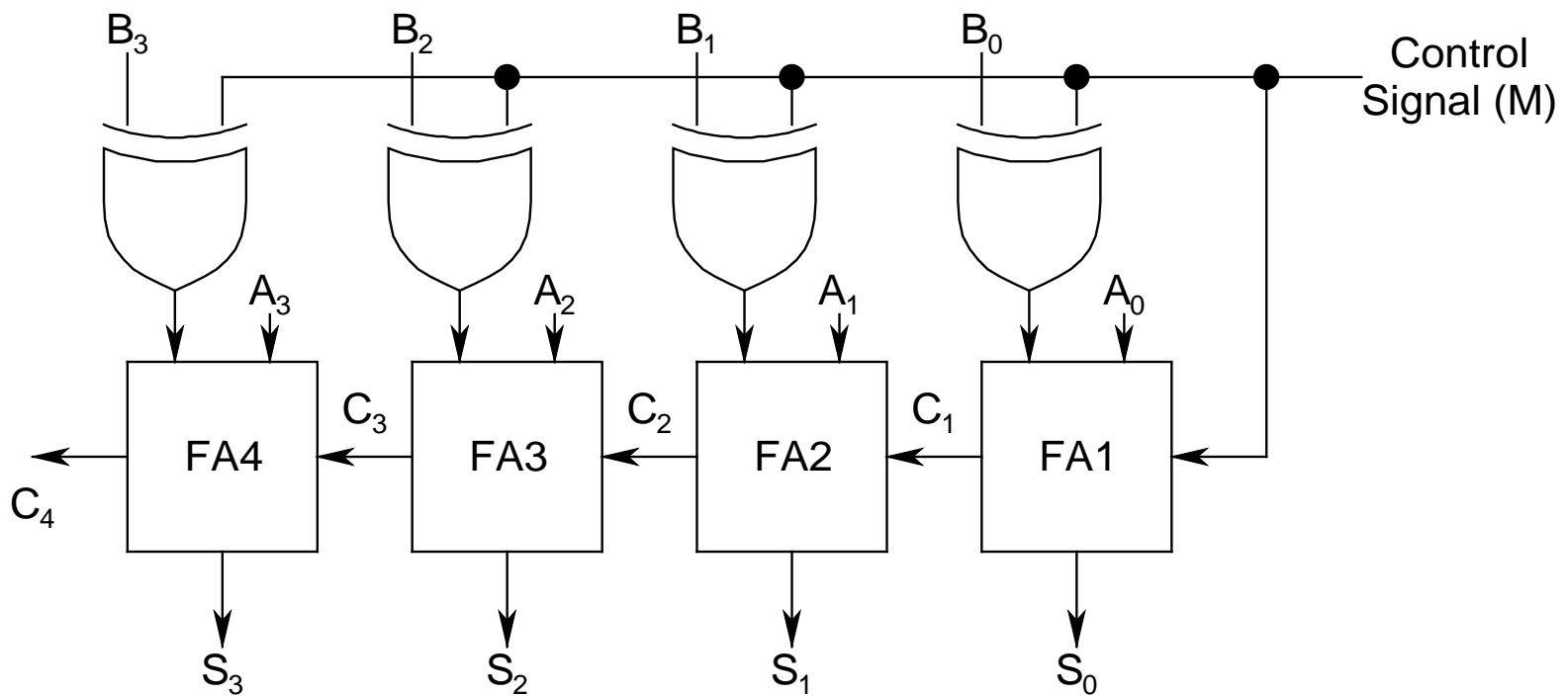* **Uses a Control Signal M** (= 0 for Adder and = 1 for Subtractor) (*Note: $1 \oplus B = B'$, $0 \oplus B = B$*)



4-Bit Adder/Subtractor (M = 0: Adder, M = 1: Subtractor)

Binary Multiplier:

* **Note:** Multiplication is an **AND** operation, i.e., the product will be 1 only if both the bits are 1

* **Example:** B_1B_0 multiplied by A_1A_0

$$\begin{array}{r}
 \begin{array}{cc} B_1 & B_0 \\ A_1 & A_0 \\ \hline A_0B_1 & A_0B_0 \\ A_1B_1 & A_1B_0 \\ \hline S_3 & S_2 & S_1 & S_0 \end{array}
 \end{array}$$

$$* S_0 = (A_0 \text{ AND } B_0)$$


$$* S_1 = (A_0 \text{ AND } B_1) \text{ ADD}$$

$(A_1 \text{ AND } B_0) \rightarrow$ can be implemented using an

Half Adder (HA)

- * $S_2 = (A_1 \text{ AND } B_1) \text{ ADD (Any Carry of } S_1)$
- * $S_3 = \text{Carry of } S_2 \rightarrow S_2 \text{ and } S_3 \text{ can be implemented by using *another HA*}$

Implementation:

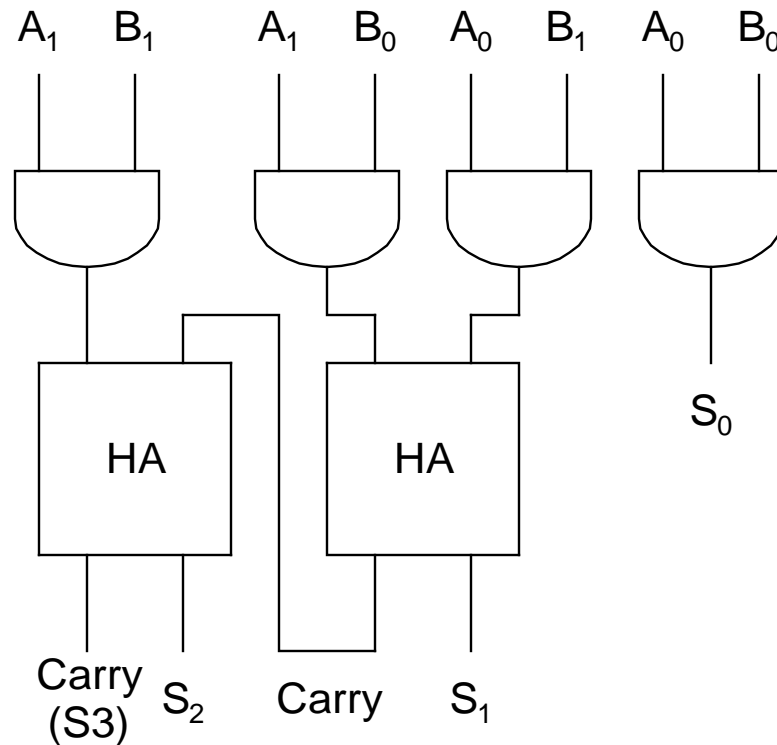


Magnitude Comparator:

- * **Compares** 2 bits A and B, and produces **3 outputs** (f_1 , f_2 , and f_3 respectively) depending on whether:
i) $A < B$, ii) $A = B$, or iii) $A > B$

i) $A < B$

B \ A	0	1
0	0	1
1	0	0


$$f_1 = A'B$$

 

ii) $A = B$

B \ A	0	1
0	1	0
1	0	1


$$f_2 = (A \oplus B)'$$

 

iii) $A > B$

B \ A	0	1
0	0	0
1	1	0

$$f_3 = AB'$$

 


Decoder:

- * **Note:** Binary code of *n bits* is capable of representing *2^n coded information*
- * Decoder is a *combinational circuit* that *converts binary information from n i/p lines to 2^n o/p lines*
- * May have *fewer than 2^n o/ps*, if some of the combinations are *unused*
- * Called **n-to-m Line Decoder**, where *$m \leq 2^n$*

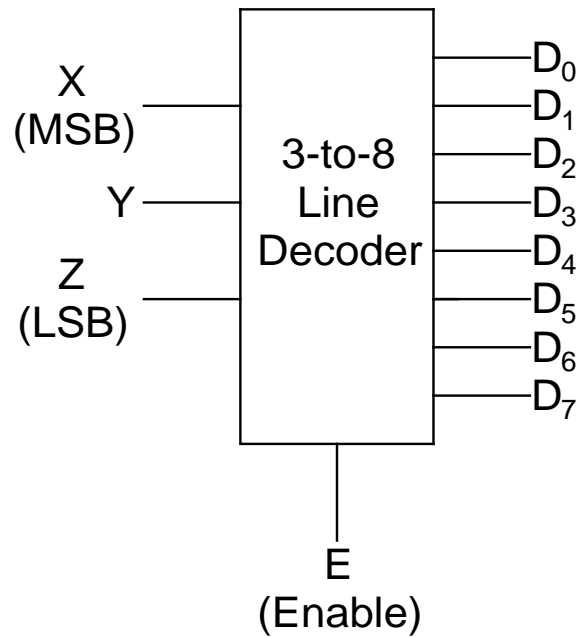* **Example: 3-to-8 Line Decoder**, where for inputs XYZ (X = MSB, Z = LSB), *one of the output lines D_0 - D_7 will go high in sequence*

- XYZ = 000, $D_0 = 1$, D_1 - $D_7 = 0$
- XYZ = 001, $D_1 = 1$, D_0 and D_2 - $D_7 = 0$
- \vdots
- XYZ = 111, $D_7 = 1$, D_0 - $D_6 = 0$



* Sometimes, uses **Enable** (E) signal: For **$E = 0$** , *all o/ps are disabled* (0), while for **$E = 1$** , the decoder circuit is *enabled*



Positive Logic:


E = 0 (Disable): all D lines 0

  E = 1 (Enable): depending on X, Y, and Z, only one of the D lines will go high



2-to-4 Line Decoder Using NAND Gates:

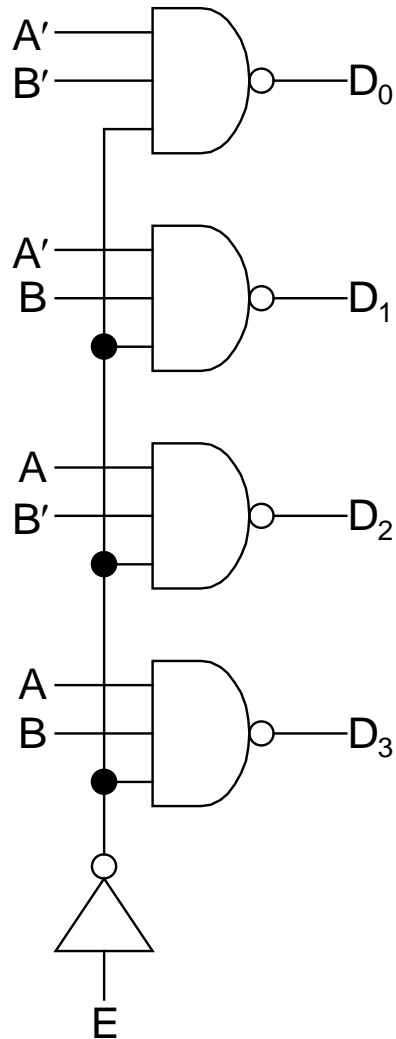- * Uses **negative logic** ($E = 0$ enables the decoder, while $E = 1$ disables it)
- * *The selected D line goes low under this case*
- * **Recall: NAND gate o/p is 0 if and only if all the inputs are 1 : If any of the i/ps is 0, o/p is 1**
- * Since $E = 0$ enables the circuit, it is also known as **Active-Low Enable Circuit**




Truth Table:

E	A	B	D_0	D_1	D_2	D_3
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

** The first row corresponds to disabled decoder with all output lines high (i/ps **DON'T CARE**)*

Constructing Large Decoders:

 Example: Construction of a **4-to-16 Line Decoder**
using two **3-to-8 Line Decoders:**



Uses positive logic: When $W = 0$, top decoder enabled and bottom decoder disabled: Outputs D_0 to D_7 correspond to $XYZ = 000$ to 111 ; and when $W = 1$, top decoder disabled and bottom decoder enabled: Outputs D_8 to D_{15} correspond to $WXYZ = 1000$ to 1111 (One of the o/p lines D_0 - D_{15} goes high depending on $WXYZ$)

Combinational Logic Implementation Using Decoders:

Example: Full Adder:


A	B	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

A \ BC _{in}				
	00	01	11	10
0	⁰ 0	¹ 1	³ 0	² 1
1	⁴ 1	⁵ 0	⁷ 1	⁶ 0

$$S = \Sigma_m(1,2,4,7)$$

A \ BC _{in}				
	00	01	11	10
0	⁰ 0	¹ 0	³ 1	² 0
1	⁴ 0	⁵ 1	⁷ 1	⁶ 1

$$C_{out} = \Sigma_m(3,5,6,7)$$

 

Full Adder Using 3-to-8 Line Decoder
(May or may not have Enable signal)

Encoder:

- * Performs *inverse* operation of a Decoder
- * Has 2^n or fewer *i/p lines*, and *n o/p lines*
- * **O/p lines generate binary code corresponding to i/p values**
- * *Only one i/p should be high, and corresponding to that i/p, only one particular o/p combination will be generated*
- * **Uses Active High logic**
- * *May or may not have Enable signal*
- * **Anomaly: When all o/ps are 0, it may be due to either the least significant i/p is 1, or all i/ps 0**

Example: Octal-to-Binary Encoder:

** Has eight i/ps (I_7 - I_0) and three o/ps (O_2 - O_0)*


I_7	I_6	I_5	I_4	I_3	I_2	I_1	I_0	O_2	O_1	O_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

* From the **Truth Table**: $O_0 = I_1 + I_3 + I_5 + I_7$,

$O_1 = I_2 + I_3 + I_6 + I_7$, and $O_2 = I_4 + I_5 + I_6 + I_7$



* **Implementation:**

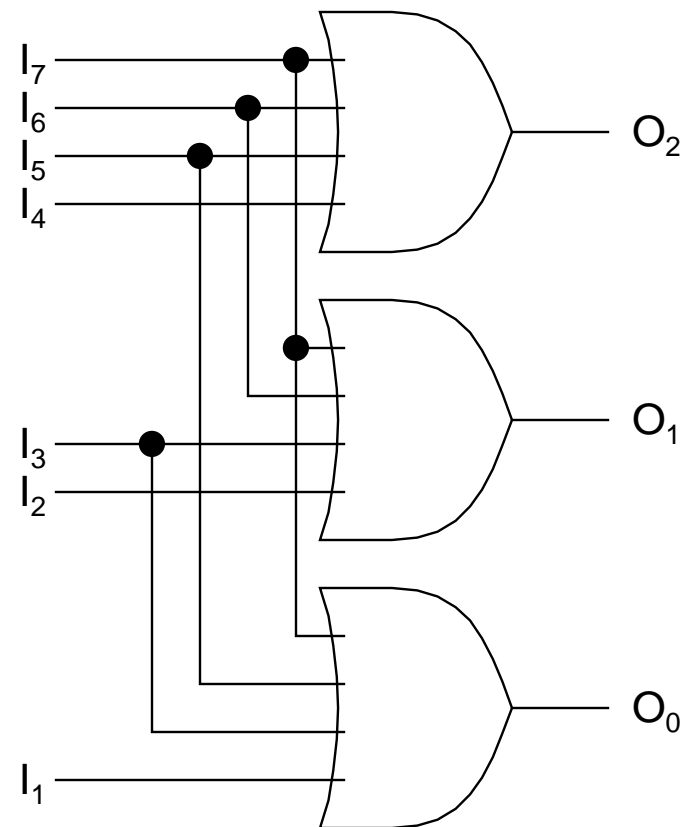I_0 : Not Used
Note: O_2 - O_0 all are 0, either
for $I_0 = 1$, or all i/ps 0
 \Rightarrow Anomaly




Multiplexer (MUX) and De-Multiplexer (De-MUX):

  * **MUX: Many-to-1**, and **De-MUX: 1-to-Many**



Multiplexer (MUX):

 - * Also known as **Data Selector**
- * *Selects binary information from one of many i/p lines and directs it to a single o/p*
- * **Needs Selection Lines to select which i/p goes to o/p**
- * 2^n i/p lines and n Selection Lines
- * **Example: 2-to-1 Line MUX:**



Boolean Function Implementation Using MUX:

- * If proper i/ps can be routed to the o/p, then a ***MUX*** can implement ***Boolean functions***
- * **Individual minterms can be selected by data i/ps**
- * ***A Boolean function having n variables can be implemented with a MUX having $(n - 1)$ Selection i/ps***

- * The first $(n - 1)$ variables of the function are connected to the Selection i/ps of the MUX**
- * *The remaining single variable of the function is used for the data i/ps***
- * If the single variable is denoted by Z , then the data i/ps of the MUX would be $Z, Z', 1$, or 0**

Example : $F(X,Y,Z) = \sum_m (1,2,6,7)$:


MSB		LSB	
X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$F = Z$$

$$F = Z'$$

$$F = 0$$

$$F = 1$$

 

Exercise: Implement


$F(A,B,C,D) =$

$\pi_M (0,2,4,5,9,13,15)$

using an 8-to-1 MUX

De-Multiplexer (De-MUX):

 - * Also known as **Data Router**
- * *Selects binary information from one i/p line and routes it to one of many o/p lines*
- * **Needs Selection lines to select the o/p line to which the i/p gets routed**
- * *2^n o/p lines and n selection lines*
- * **(Decoder + Enable) \leftrightarrow De-MUX**



Example : 1-to-4 De-MUX:



S_1 S_0 I goes to

0 0 O_0

0 1 O_1


1 0 O_2

1 1 O_3

  


Higher-Order De-MUX:

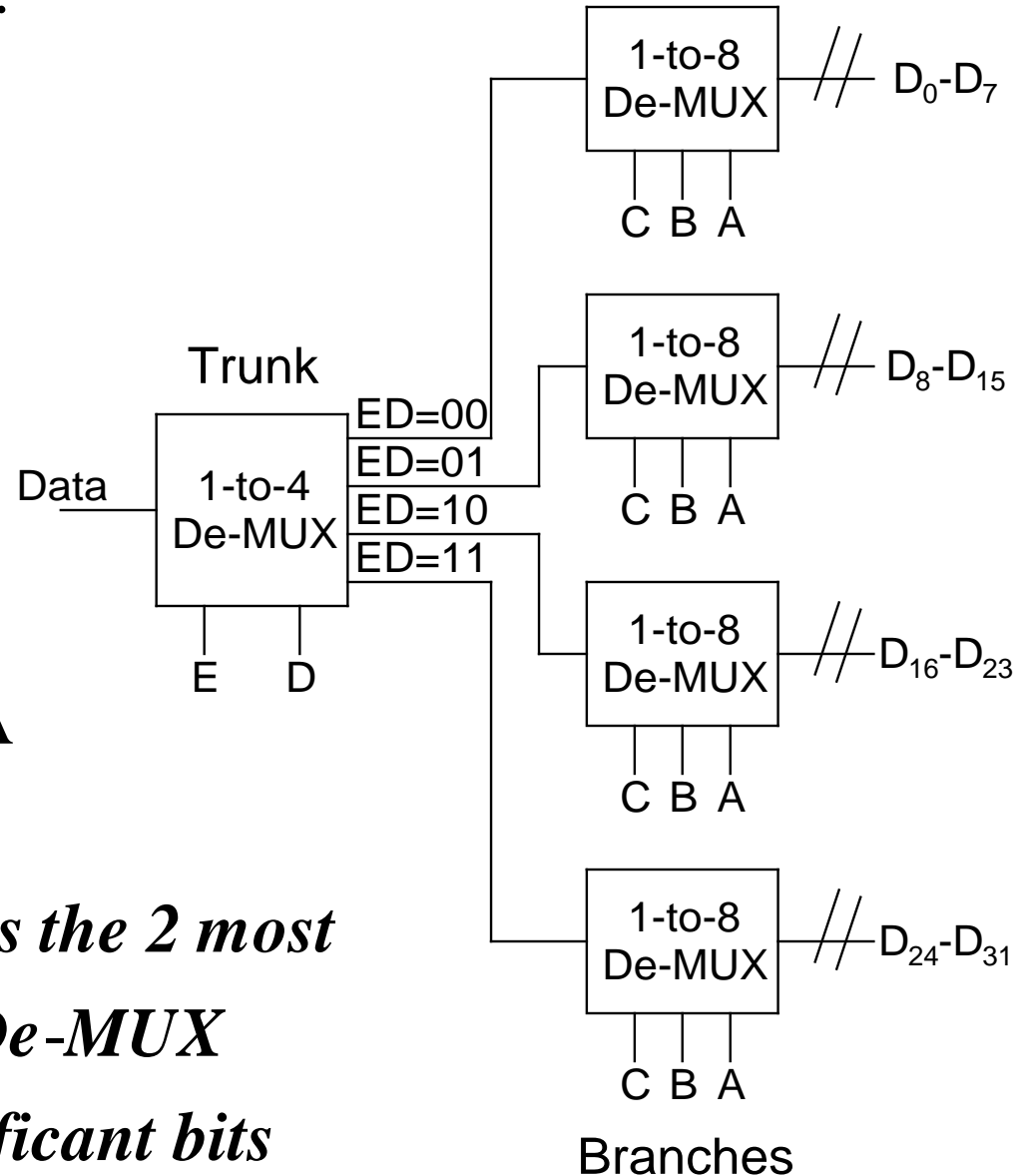- * Construction of a **1-to-32 De-MUX** using **1-to-4** and **1-to-8 De-MUX**
- * *Trunk and Branches Architecture*
- * **Control Signal: EDCBA**
(E: MSB, A: LSB)
- * *1-to-4 De-MUX controls the 2 most significant bits, 1-to-8 De-MUX control the 3 least significant bits*




Decoder as De-MUX & Vice-Versa:

 

1-to-4 De-MUX as
2-to-4 Decoder

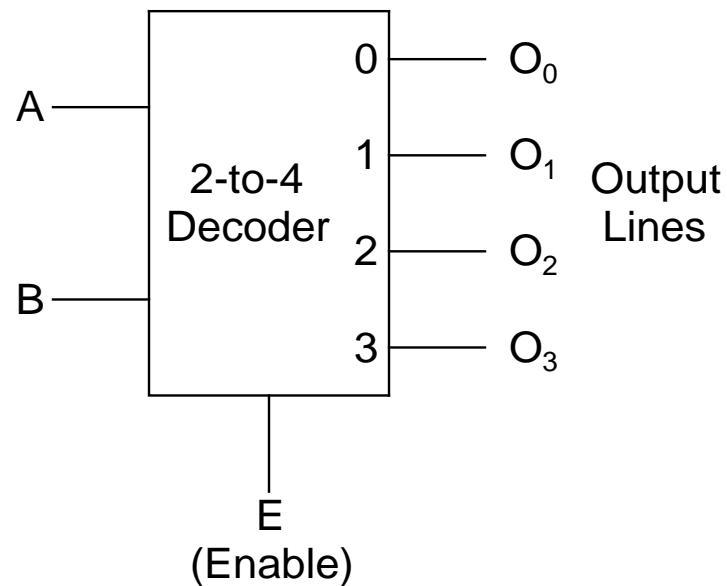- * Use the i/p line (I) as the **Enable (E)** signal
- * *Use the Select lines (S_1 - S_0) as the i/p lines of the decoder*
- * **When I (or E) = 0, all o/ps 0**
- * **When I (or E) = 1:**
 - $S_1 S_0 = 00, O_0 = 1, \text{all others } 0$
 - $S_1 S_0 = 01, O_1 = 1, \text{all others } 0$
 - $S_1 S_0 = 10, O_2 = 1, \text{all others } 0$
 - $S_1 S_0 = 11, O_3 = 1, \text{all others } 0$



2-to-4 Decoder as
1-to-4 De-MUX

*** Use Enable (E) line
as the i/p line (I)**

*** *Use the i/ps (A and B)
as Select lines (S_1 - S_0)***

*** When E (or I) = 0, all o/ps 0**

*** When E (or I) = 1:**

• $AB = 00, O_0 = 1, \text{all others } 0$

• $AB = 01, O_1 = 1, \text{all others } 0$

• $AB = 10, O_2 = 1, \text{all others } 0$

• $AB = 11, O_3 = 1, \text{all others } 0$