

CS220A Lab#5

Rotary Shaft Encoder

Mainak Chaudhuri
Indian Institute of Technology Kanpur

Sketch

- Assignment#1: rotary shaft encoder

Lab#5

- Make a new folder Lab5_1 under CS220Labs to do the assignment
- Refer to lab#1 slides for Xilinx ISE instructions
- Finish pending assignments from lab#4 first
- Three marks for this assignment

Assignment#1

- Rotary shaft encoder
 - The rotary shaft can rotate in both directions and while rotating it generates two input signals ROT_A and ROT_B
 - Read pages 18 and 19 of https://www.xilinx.com/support/documentation/boards_and_kits/ug230.pdf
 - Figure 2.8 shows how ROT_A and ROT_B signals change as the shaft makes right rotation i.e., A becomes HIGH first and then B becomes HIGH
 - If you read Figure 2.8 from right hand side, it shows what happens when the shaft rotates left i.e., B goes HIGH first and then A goes HIGH

Assignment#1

- Rotary shaft encoder
 - One rotation event is referred to as rotating the shaft to left or right by one step
 - Several steps constitute one full 360° rotation
 - Figure 2.8 shows that one step rotation to the right from detent position (stationary shaft position) causes ROT_A to go HIGH first and then ROT_B goes HIGH
 - Similarly, one step rotation to the left from detent position causes ROT_B to go HIGH first and then ROT_A goes HIGH
 - The changing voltages on ROT_A and ROT_B arise from closing/opening of two mechanical switches
 - These switches suffer from “chatter” i.e., they bounce for a while before settling; leads to train of narrow pulses in ROT_A and ROT_B before they stabilize

Assignment#1

- Rotary shaft encoder
 - The goal of the assignment is to write a Verilog module that can correctly capture every rotation event and the associated direction
 - At a very high level, a rotation event can be captured by observing the changing levels in ROT_A or ROT_B
 - The challenge is to filter out the chatters so that a false rotation event is not detected (i.e., your module detects a rotation when there is actually no rotation)
 - The direction of a rotation can be detected by understanding the relative order of change in ROT_A and ROT_B
 - The challenge here again is to filter out the chatters

Assignment#1

- Rotary shaft encoder
 - On detecting a rotation event, depending on the direction of the rotation, an LED ripple makes one step progress in the direction of the rotation
 - Structure of the Verilog module
 - Inputs: clk, ROT_A, ROT_B
 - Use the clock generated from pin C9 as you did in lab#3
 - Outputs: rotation_event, rotation_direction (both reg)
 - On posedge clk
 - If ROT_A and ROT_B both are 1, set rotation_event to 1
 - If ROT_A and ROT_B both are 0, set rotation_event to 0
 - If ROT_A is 0 and ROT_B is 1, set rotation_direction to 1
 - If ROT_A is 1 and ROT_B is 0, set rotation_direction to 0₇

Assignment#1

- Rotary shaft encoder
 - Observe from Figure 2.8 that `rotation_direction == 1` means left rotation and `rotation_direction == 0` means right rotation
 - Observe that a rising edge in `rotation_event` signifies a step of rotation
 - Observe that sampling `rotation_direction` at the time of a rising edge in `rotation_event` can tell us the direction of rotation
 - Write another Verilog module which exploits these observations to drive LED ripples in appropriate directions

Assignment#1

- Rotary shaft encoder
 - Structure of the second Verilog module
 - Inputs: clk, rotation_event, rotation_direction
 - Outputs: led0, led1, led2, led3, led4, led5, led6, led7
 - Similar to rippling LED assignment from lab#3
 - Initialize at least one LED to 1
 - On posedge clk
 - Copy rotation_event to prev_rotation_event (a local reg initialized to 1) i.e., `prev_rotation_event <= rotation_event`
 - If prev_rotation_event is 0 and rotation_event is 1 (indicates a rising edge in rotation_event)
 - » If rotation_direction is 0, shift LEDs to right i.e., `led0 <= led1, led1 <= led2, ..., led6 <= led7, led7 <= led0`
 - » If rotation_direction is 1, shift LEDs to left i.e., `led1 <= led0, led2 <= led1, ..., led7 <= led6, led0 <= led7`

Assignment#1

- Rotary shaft encoder
 - Write a top-level Verilog module with inputs clk, ROT_A, ROT_B and outputs led0, ..., led7
 - Instantiates the previous two Verilog modules and establishes the connection between them
 - Use PlanAhead to assign pins to the inputs and outputs of the top-level module
 - Synthesize the hardware
 - No need to simulate this design in ISim because ROT_A and ROT_B cannot be given exact input behavior as they will receive from the rotary shaft